

--	--	--	--	--	--	--	--	--	--

B. TECH.
(SEM IV) THEORY EXAMINATION 2022-23
DIGITAL ELECTRONICS

*Time: 3 Hours**Total Marks: 100***NOTE: 1.** Attempt all Sections. If require any missing data, then choose suitably.

SECTION A

1. Attempt all questions in brief.**2 x 10 = 20**

- (a) Interpret the binary number $(1011)_2$ into (i) Gray code (ii) Excess-3 Code.
- (b) Evaluate $(1011)_2 - (1101)_2$ using 1's and 2's complement method.
- (c) Differentiate between the serial and parallel adder.
- (d) How many 4 X 1 multiplexers are required to implement 64 X 1 multiplexer.
- (e) What is the difference between characteristic and excitation table.
- (f) Differentiate between combinational and sequential circuits.
- (g) How many address lines are needed to represent 8K meaning.
- (h) Define term propagation delay.
- (i) Define race around condition in JK flip flop.
- (j) Give the difference between PAL and PLA.

SECTION B

2. Attempt any three of the following:**10x3=30**

- (a) Implement the Boolean function $F(x,y,z)=(1,2,3,4,6,7)$ using NAND gates.
- (b) Construct a full adder and implement the full adder with the help of half adders. Also implement the full adder with NAND gates only.
- (c) Discuss excitation table for SR, JK, T and D flip flop.
- (d) Design 8Kx8 RAM memory system, using 1Kx8 memory ICs.
- (e) Discuss Mealy and Moore finite state machine with an example.

SECTION C

3. Attempt any one part of the following:**10x1=10**

- (a) Simplify $Y = \sum m(3,6,7,8,10,12,14) + d(0,1,6,15)$ using K-map method and implement the simplified circuit using logic gates.
- (b) Minimize the following Boolean function using tabulation method:
 $F(a,b,c,d,e) = \sum m(0,4,12,16,19,24,27,28,29,31)$

4. Attempt any one part of the following:**10x1=10**

- (a) Design a BCD adder using 4-bit parallel adder.
- (b) Draw and Explain 2-bit magnitude comparator. Also represent output with the help of logic diagram.

5. Attempt any *one* part of the following: 10x1=10

- (a) Design and implement MOD-10 synchronous counter.
- (b) For the clocked JK Flip-Flop write the state table, state equation with state diagram.

6. Attempt any *one* part of the following: 10x1=10

- (a) Why ECL is better? Implement NAND gate with DTL and TTL.
- (b) Define noise margin, Fan-in, Fan-out as characteristics of logic families. Implement NAND gate with CMOS.

7. Attempt any *one* part of the following: 10x1=10

- (a) Explain State Reduction and assignment with suitable example.
- (b) Design a sequential circuit with two flip flops, A & B and one input X. When X=0 state of the circuit remains the same, when X =1 circuit passes through the state transition from 00 to 01 to 11 to 10 back to 00 and repeat.

QP23EP2_290
| 03-08-2023 13:26:30 | 117.55.242.132