

END TERM EXAMINATION

FOURTH SEMESTER [B.TECH] JUNE 2025

Paper Code: EEC-208

Subject: Circuits and Systems

Time: 3 Hours



Maximum Marks: 60

Note: Attempt five questions in all including Q.No.1 which is compulsory. Select one question from each unit. Assume missing data, if any.

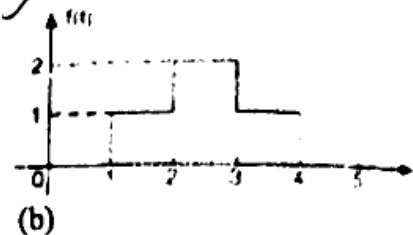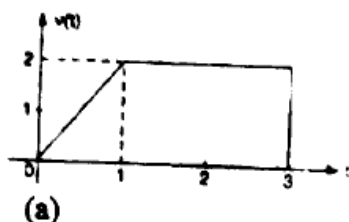Q1 Attempt any four of the following questions:

(4×5=20)


- Define and classify signals with suitable examples.
- State and explain Laplace Transform properties.
- Derive the differential equation of an RLC series circuit.
- Obtain the Laplace transform of $e^{-at}\sin\omega t$ and $1-e^{-at}$ where a is constant.
- Synthesize the waveforms:



- Define and explain two-port parameters.
- What are the key differences between z-Transform and Laplace Transform?
- Explain any two properties of network functions.

UNIT-I

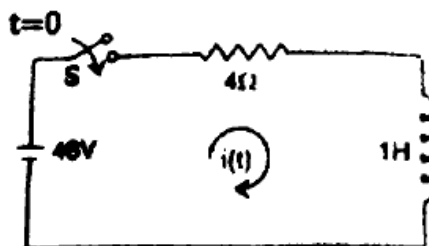- Q2
- Define LTI systems and discuss their characteristics. (5)
 - Consider the R-L circuit with $R=4\Omega$ and $L=1H$ excited by a 48V d.c. source as shown in figure. Assume the initial current through the inductor is 3A. Using the Laplace transform determine the current $i(t)$; $t \geq 0$. Also draw the s-domain representation of the circuit. (5)



OR

- Q3
- Explain the concept of state space analysis with an example. (5)
 - Discuss the properties of z-Transform. (5)

UNIT-II


- Q4
- Find the transient response of an RLC circuit for a step input using Laplace Transform. (5)
 - Determine $f(0+)$ and $f(\infty)$ for the following function: (5)

$$F(s) = \frac{5s^3 - 1600}{s(s^3 + 18s^2 + 90s + 800)}$$

P.T.O

OR

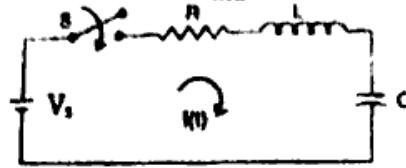- Q5 a) Consider the RLC series circuit shown in figure. $V_s = 2V$; $R = 6\Omega$; $L = 2H$; $C = 0.25F$. Determine $i(0^+)$; $\frac{di}{dt}(0^+)$; $\frac{d^2i}{dt^2}(0^+)$ and $i(t)$. (5)




- b) Without finding the inverse Laplace transform of $F(s)$, determine $f(0^+)$ and $f(\infty)$ for each of the following functions: (5)

(i) $F(s) = \frac{4e^{-2s}(s+50)}{s}$ (ii) $F(s) = \frac{s^2+6}{s^2+7}$

UNIT-III

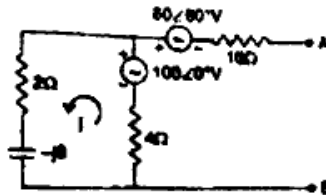
- Q6 a) Find the Thevenin's equivalent circuit at terminals AB of the given circuit. (5)



- b) Explain the Y- Δ (Star-Delta) and Δ -Y (Delta-Star) transformations. Provide the formulas used for the conversion. (5)

OR

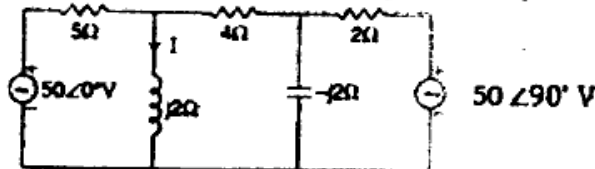- Q7 a) State and explain Thevenin's and Norton's theorems. How are these theorems applied to simplify complex AC circuits? (5)
 b) Find current I in the circuit using mesh analysis. <https://www.ggsipuonline.com> (5)



UNIT-IV

- Q8 a) Define ABCD parameters and explain their significance. (5)
 b) Derive the condition for reciprocity and symmetry in case of (a) T parameters and (b) h parameters (5)

OR

- Q9 a) Obtain the Z parameters of the network in terms of ABCD and hybrid parameters. (5)
 b) Explain how Hurwitz polynomial is used in network analysis. (5)
