

(Please write your Exam Roll No.)

Exam Roll No.

END TERM EXAMINATION

FOURTH SEMESTER [B.TECH] JUNE 2025

Paper Code: ECC-218

Subject: Electronics-II

Time: 3 Hours

Maximum Marks: 60

Note: Attempt all questions as directed. Internal Choice is indicated.

- Q1 Attempt **any four** of the following questions: (4x5=20)
- (a) Explain the concept of Heat Sink in detail required for Power Amplifiers.
 - (b) Sketch Symbol of n-channel and p-channel Depletion MOSFET. State giving reasons, why it is known as depletion MOSFET?
 - (c) Explain the working of operational amplifier as summer.
 - (d) Draw the block diagram of current series and current shunt feedback amplifier.
 - (e) Explain the effect of feedback on gain, bandwidth and noise.
 - (f) Define efficiency for a Power Amplifier and write the expression for the same. State the efficiency of Class A, Class B and Class C Amplifiers respectively.
 - (g) State and explain Barkhausen's Criteria.
 - (h) Write a short notes on Darlington pair amplifier.

UNIT-I

- Q2 Design a two stage RC coupled CS - CE Amplifier to meet following specifications: $A_v \geq 750$, $S \leq 10$, $R_i \geq 1 \text{ M}\Omega$, $V_{cc} = 10 \text{ V}$. Assume the following data: $\beta_{typ} = 290$, $h_{ie} = 4.5 \text{ k}\Omega$, $g_{m0} = 5000 \mu\text{S}$, $I_{DSS} = 7 \text{ mA}$, $r_d = 50 \text{ k}\Omega$, $V_P = -4 \text{ V}$. (10)

OR

- Q3 Sketch Circuit Diagram, AC equivalent Model and Derive expressions for Input impedance, Output Impedance, Voltage Gain and Current Gain of a two stage CE Amplifier. (10)

UNIT-II

- Q4 For a 'n' stage cascaded amplifier, show that overall lower 3 dB cut - off frequency is $f_{LT} = \frac{f_L}{\sqrt{(2)^{\frac{1}{n}} - 1}}$ and overall higher frequency is

$$f_H' = f_H \left(\sqrt{(2)^{\frac{1}{n}} - 1} \right).$$

(10)

OR

- Q5 Draw a neat diagram of Class AB power Amplifier and explain its working. (10)

UNIT-III

- Q6 Draw RC phase shift oscillator using BJT and derive the frequency of oscillation for same. (10)


P.T.O.

[-2-]

OR

Q7 Determine the output of the circuit given in the figure:

(10)

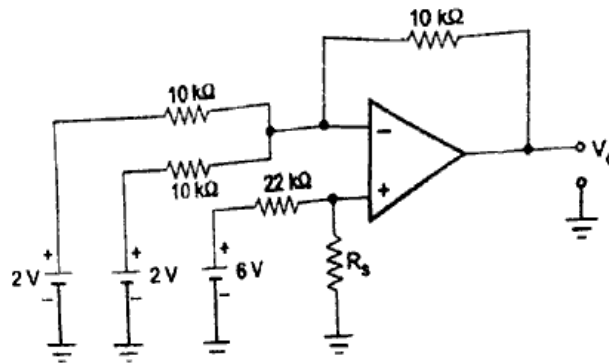

UNIT-IV

Q8 (a) Compare Small Signal and Large Signal amplifier. **(5)**

(b) Calculate frequency of Oscillation for Hartley Oscillator if $L_1 = 5\text{mH}$,
 $L_2 = 2\text{mH}$ and $C = 0.5\text{ }\mu\text{F}$. **(5)**

OR

Q9 Explain the working of astable multivibrator using 555 IC. **(10)**
