

END TERM EXAMINATION

FOURTH SEMESTER [B.TECH] JUNE 2025

Paper Code: EEC-206

Subject: Network Analysis and Synthesis

Time: 3 Hours

Maximum Marks: 60

Note: Attempt any five questions including Q.No.1 which is compulsory. Select one question from each unit.

Q1 Attempt **ALL PARTS**

[4x5=20]

- a) Differentiate between f-cut sets and f-tie sets.
 b) Synthesis the following waveforms using gate function:

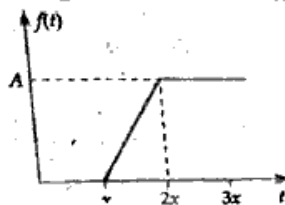


Fig: 1

- c) Determine ABCD parameters in terms of Z-parameters.
 d) Check the positive realness of the function $Y(s) = \frac{s^2 + 2s + 20}{s + 10}$
 e) Differentiate between causal and non-causal systems.

UNIT-I

- Q2 a) For the graph shown in fig: 2, consider tree formed by branches (1, 2, 5), using this tree write A_c , A , B_f and Q_f . [10]

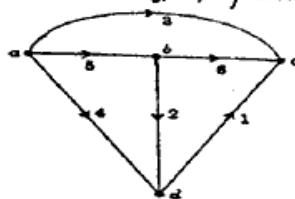


Fig: 2

- Q3 Find the drop across 2Ω resistor in the network of Fig: 3 using mesh analysis. [10]

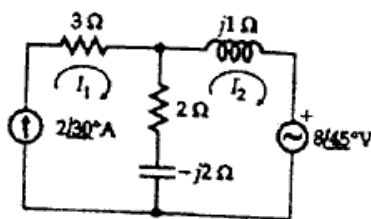


Fig: 3

UNIT-II

- Q4 In a series R-L circuit, the application of a direct voltage results a steady state current of $0.632I$ in 1 second. I being the final steady state value of the current. However, after the current has reached its final value, a sudden short circuit is applied against the source. What would be the current after one second?

[10]

P.T.O.

Q5 Derive the expression for initial value and final value theorem. [10]

Unit - III

Q6 Obtain the h-parameters of fig: 4? [10]

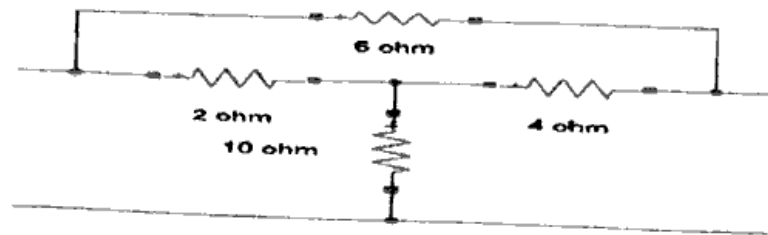


Fig IV

Q7 a) Drive input and output impedance in terms of ABCD-parameters.
b) Briefly Drive the expression parallel-parallel connection. [5,5]

UNIT-IV

Q8 Synthesize the network having driving point impedance $Z(s) = \frac{2s^5 + 10s^3 + 10s}{s^4 + 4s^2 + 3}$ in the Cauer's form. [10]

Q9 Write a short note on
a) Low pass filter
b) High pass filter [5,5]
