

(Please write your Exam Roll No.)

Exam Roll No.

END TERM EXAMINATION

THIRD SEMESTER [B.TECH] DECEMBER 2024

Paper Code: ECC-215

Time: 3 Hours

Subject: Electronics-I

Maximum Marks: 60

Note: Attempt all questions as directed. Internal choice is indicated.

- Q1 Attempt any Four of the following Questions. (4x5=20)
- (a) Draw the energy band for Metal, Semiconductor and Insulator.
 - (b) Write the difference between Direct band semiconductor and Indirect band semiconductor.
 - (c) A diode has leakage current of $5\mu\text{A}$ at 10°C . Find its value when the temperature is 35°C .
 - (d) Write short notes on Zener diode and draw the V-I characteristics.
 - (e) Draw and write the operation of npn transistor in active region.
 - (f) Reduce the following Boolean function using Boolean algebra.
$$F = AB + \bar{A}B + BC$$
 - (g) Draw and explain the Full Adder.
 - (h) Write the difference between Synchronous Counter and Asynchronous Counter.
- Q2 A pure semiconductor (Ge) is doped with donor impurities to the extent of 10^7 . Find Donor concentration, Electron concentration, Hole concentration And Conductivity of the doped semiconductor. (10)
(Assume: Total number of atoms in Ge is $4.4 \times 10^{23} \text{ cm}^{-3}$. $n_i = 2.5 \times 10^{13} \text{ Atom/cm}^{-3}$, $\mu_n = 3800 \text{ cm}^2/\text{V-Sec}$, $\mu_p = 1800 \text{ cm}^2/\text{V-Sec}$).
- OR
- Q3 Explain working of Tunnel diode with V-I characteristics and suitable diagrams. (10)
- Q4 Explain Half wave rectifier and full wave rectifier with suitable circuit diagram and waveform. (10)
- OR
- Q5 Explain working of Common Emitter (CE) configuration of npn transistor with suitable diagrams. Also draw the input and output characteristics. (10)
- Q6 Write the operation of N-Channel enhancement MOSFET and depletion MOSFET with suitable block diagram and V-I characteristics. (10)
- OR
- Q7 Reduce the following Boolean function using K-map. (10)
$$f(A, B, C, D) = \sum m(0, 1, 3, 5, 9, 11, 13) + \sum d(7, 10, 15)$$
- Q8 Draw and explain Carry Look-ahead Adder in detail. (10)
- OR
- Q9 What is J-K Flip-flop? What is Race around condition in J-K flip-flop and how it can overcome? (10)
- *****