

# END TERM EXAMINATION

THIRD SEMESTER [B.TECH] DECEMBER 2024-JANUARY 2025

Paper Code: ECC-211

Subject: Analog Electronics-I

Time: 3 Hours

Maximum Marks: 60

**Note: Attempt five questions in all including Q. No.1 which is compulsory. Select one question from each unit. Assume missing data, if any.**

Q1 Attempt all questions:-

(5x4=20)

- (a) Draw a Darlington pair and find out its current gain.
- (b) Explain how Zener diode maintains constant voltage across the load?
- (c) The output of a 60 Hz full wave bridge rectifier has a 60 Hz ripple. Is the circuit working properly.
- (d) Why emitter is always forward biased? Why collector is always reverse biased w.r.t base.
- (e) An amplifier with voltage gain of 60 dB uses 1/20 of its output in negative feedback. Calculate the gain with feedback in dB.
- (f) A transformer coupled class A large signal amplifier has maximum and minimum values of collector-emitter voltage of 25V and 2.5V. Determine its collector efficiency?

## UNIT-I

- Q2 (a) Draw the piecewise linear equivalent circuit of diode and explain it briefly. Explain the effect of temperature on the V-I characteristics of diode. (4)
- (b) In a centre tap full wave rectifier  $R_L = 1000 \text{ ohm}$ ,  $R_f = 35 \text{ ohm}$ . Primary voltage is 220V 50Hz with transformer ratio 5:1. Calculate (i) Average current (ii) d.c output voltage (iii) d.c output power (iv) a.c input power and (v) rectifier efficiency. (3)
- (c) What are the two basic types of capacitances associated with P-N junction? Explain them. (3)

## OR

- Q3 (a) A voltage across a silicon diode at room temperature of 300K is 0.71V when 2.5 mA current flows through it. If the voltage increases to 0.8V, calculate the new diode current. (2)
- (b) Draw the circuit diagram of a bridge rectifier and explain its operation with waveforms. Derive expression for its rectification efficiency and ripple factor. (4)
- (c) Design a clipping circuit to clip a sinusoidal wave of 2V peak voltage at 100 Hz above +1 volt. Draw input and output waveforms. (4)

## UNIT-II

- Q4 (a) What is self bias? Derive the expression for stability factor  $S(I_{co})$  for self bias circuit. Draw the graph of variation of  $S(I_{co})$  with change in  $R_B/R_E$ . (5)
- (b) Draw the hybrid equivalent circuit for common emitter configuration and find expression for current gain, voltage gain, input impedance, output impedance. (5)

## OR

- Q5 (a) Design a self bias circuit for C.E. amplifier having  $\beta=99$  and stability  $S=5$ . The other values are  $V_{CE} = 6V$ ,  $V_{RE} = 5.5V$ ,  $V_{CC} = 15V$ ,  $R_C = 2.5k$  ohm and  $V_{BE}=0.3V$ . (5)
- (b) Draw the structure of an N- channel enhancement type MOSFET. Explain it's working with the help of drain characteristics and transfer characteristics. (5)

### UNIT-III

- Q6 (a) Discuss class B power amplifier and calculate its overall efficiency. (5)
- (b) A class B push pull amplifier is supplied with  $V_{CC}=50V$ . The signal swings the collector voltage down to  $V_{min}=5V$ . The total dissipation in both transistors is 40W. Find the total power and conversion efficiency. (5)

**OR**

- Q7 (a) Draw the circuit diagram of two stage R-C coupled amplifier. Derive an expression for the voltage gain in mid-frequency region. (5)
- (b) Explain the need for a multistage amplifier. Draw the circuit of a cascode amplifier and explain its operation. (5)

### UNIT-IV

- Q8 (a) Why is negative feedback involved in high gain amplifiers. Prove in a negative feedback amplifier  $\frac{dA_f}{A_f} = \frac{1}{1+\beta A} \frac{dA}{A}$  where  $A_f$  is Gain with feedback,  $A$  is gain without feedback and  $\beta$  is feedback factor. (5)
- (b) What is piezoelectric effect? Draw the equivalent electric circuit of a quartz crystal and find the expression for resonant frequencies. (5)

**OR**

- Q9 (a) Explain the four types of feedback topologies with the help of schematic diagram. (6)
- (b) Describe Hartley oscillator circuit and explain its action. (2)
- (c) Find the operating frequency of a transistor Collpitt's oscillator if  $C1=0.001\mu F$ ,  $C2=0.01\mu F$  and  $L=15\mu H$ . (2)

\*\*\*\*\*

<https://www.ggsipuonline.com>

Whatsapp @ 9300930012

Send your old paper & get 10/-

अपने पुराने पेपर्स भेजे और 10 रुपये पायें,

Paytm or Google Pay से